

1. RMS stands for \_\_\_\_\_
  - (a) **Root Mean Square**
  - (b) Root Mean Sum
  - (c) Root Maximum sum
  - (d) Root Minimum Sum
  
2. What is the effective value of current?
  - (a) **RMS current**
  - (b) Average current
  - (c) Instantaneous current
  - (d) Total current
  
3. In a sinusoidal wave, average current is always \_\_\_\_\_ rms current.
  - (a) Greater than
  - (b) **Less than**
  - (c) Equal to
  - (d) Not related
  
4. For a rectangular wave, average current is \_\_\_\_\_ rms current.
  - (a) Greater than
  - (b) Less than
  - (c) **Equal to**
  - (d) Not related
  
5. Peak value divided by the rms value gives us?
  - (a) Peak factor
  - (b) Crest factor
  - (c) **Both (a) and (b)**
  - (d) Neither peak nor crest factor
  
6. If maximum value of current is  $5\sqrt{2}$  A, what will be the value of RMS current?
  - (a) 10 A
  - (b) **5 A**
  - (c) 15 A
  - (d) 25 A

7. If  $I_m$  is the maximum value of a sinusoidal voltage, what is the instantaneous value?
- (a)  $i = I_m/2$
  - (b)  $i = I_m \sin \theta$
  - (c)  $i = I_m \cos \theta$
  - (d)  $i = I_m \sin \theta$  or  $i = I_m \cos \theta$**
8. Average value of current over a half cycle is?
- (a)  $0.67 I_m$**
  - (b)  $0.33 I_m$
  - (c)  $6.7 I_m$
  - (d)  $3.3 I_m$
9. What is the correct expression for the form factor?
- (a)  $I_{rms} * I_{av}$
  - (b)  $I_{rms} / I_{av}$**
  - (c)  $I_{rms} + I_{av}$
  - (d)  $I_{rms} - I_{av}$
10. For a direct current, the rms current is \_\_\_\_\_ the mean current.
- (a) Greater than
  - (b) Less than
  - (c) Equal to**
  - (d) Not related to
11. What is the value of the form factor for sinusoidal current?
- (a)  $\pi/2\sqrt{2}$**
  - (b)  $\pi/4$
  - (c)  $2\pi$
  - (d)  $\pi/\sqrt{2}$
12. In Series RLC circuit, phase difference between voltage across inductor and capacitor is
- (a) Zero
  - (b)  $\pi/2$
  - (c)  $\pi$**
  - (d)  $2\pi$

13. The number of complete cycles of an alternating current occurring in one second is known as:
- (a) the maximum value of the alternating current
  - (b) the frequency of the alternating current**
  - (c) the peak value of the alternating current
  - (d) the r.m.s. or effective value
14. The value of an alternating current at any given instant is:
- (a) a maximum value
  - (b) a peak value
  - (c) an instantaneous value**
  - (d) an r.m.s. value
15. An alternating current completes 100 cycles in 0.1 s. Its frequency is:
- (a) 20 Hz
  - (b) 100 Hz
  - (c) 0.002 Hz
  - (d) 1 kHz**
16. The value normally stated when referring to alternating currents and voltages is the:
- (a) instantaneous value
  - (b) r.m.s. value**
  - (c) average value
  - (d) peak value
17. State which of the following is false. For a sine wave:
- (a) the peak factor is 1.414
  - (b) the r.m.s. value is  $0.707 \times \text{peak value}$
  - (c) the average value is  $0.637 \times \text{r.m.s. value}$**
  - (d) the form factor is 1.11
18. The period of a wave is
- (a) the same as frequency
  - (b) time required to complete one cycle**
  - (c) expressed in amperes
  - (d) none of the above

19. The period of a sine wave is  $1/50$  Its frequency is
- (a) 20 Hz
  - (b) 30 Hz
  - (c) 40 Hz
  - (d) 50 Hz**
20. The maximum instantaneous value measured from zero value is known as?
- (a) Peak value**
  - (b) Peak to peak value
  - (c) Cycle
  - (d) Period
21. Power in a Three Phase Circuit = \_\_\_\_\_.
- (a)  $P = 3 V_{ph} I_{ph} \cos\Phi$
  - (b)  $P = \sqrt{3} V_L I_L \cos\Phi$
  - (c) Both a & b.**
  - (d) None of The Above
22. In a three phase AC circuit, the sum of all three generated voltages is \_\_\_\_\_
- (a) Infinite ( $\infty$ )
  - (b) Zero (0)**
  - (c) One (1)
  - (d) None of the above
23. For a star connected three phase AC circuit \_\_\_\_\_
- (a) Phase voltage is equal to line voltage and phase current is three times the line current
  - (b) Phase voltage is square root three times line voltage and phase current is equal to line current
  - (c) Phase voltage is equal to line voltage and line current is equal to phase current
  - (d) None of the above**
24. In a three phase, delta connection \_\_\_\_\_
- (a) line current is equal to phase current
  - (b) Line voltage is equal to phase voltage**
  - (c) None of the above
  - (d) Line voltage and line current is zero

25. The angular displacement of three phase voltage is


- (a) zero
- (b)  $90^\circ$
- (c)  **$120^\circ$**
- (d)  $180^\circ$

26. In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V \angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{YB}$  is?

- (a)  $V \angle 0^\circ$
- (b)  **$V \angle -120^\circ$**
- (c)  $V \angle 120^\circ$
- (d)  $V \angle 240^\circ$

27. In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V \angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{BR}$  is?

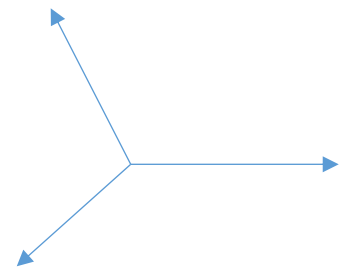- (a)  $V \angle 180^\circ$
- (b)  $V \angle 240^\circ$
- (c)  **$V \angle -240^\circ$**
- (d)  $V \angle -120^\circ$



28. In a three-phase system, when the loads are perfectly balanced, the neutral current is

- (a) **zero**
- (b) one-third of maximum
- (c) two-thirds of maximum
- (d) at maximum

29.