

# Nepal Engineering Council Registration Examination Preparation Class

## Computer Engineering

### 1.5 Signal Generator

## **1. Concept of Basic Electrical and Electronics Engineering**

**(AExE01)**

**1.1 Basic concept:** Ohm's law, electric voltage current, power and energy, conducting and insulating materials. Series and parallel electric circuits, star-delta and delta-star conversion, Kirchhoff's law, linear and non-linear circuit, bilateral and unilateral circuits, active and passive circuits.

**1.2 Network theorems:** concept of superposition theorem, Thevenin's theorem, Norton's theorem, maximum power transfer theorem. R-L, R-C, R-L-C circuits, resonance in AC series and parallel circuit, active and reactive power.


**1.3 Alternating current fundamentals:** Principle of generation of alternating voltages and currents and their equations and waveforms, average, peak and rms values. Three phase system.

**1.4 Semiconductor devices:** Semiconductor diode and its characteristics, BJT Configuration and biasing, small and large signal model, working principle and application of MOSFET and CMOS.

**1.5 Signal generator:** Basic Principles of Oscillator, RC, LC and Crystal Oscillators Circuits. Waveform generators.

**1.6 Amplifiers:** Classification of Output Stages, Class A Output Stage, Class B Output Stage, Class AB Output Stage, Biasing the Class AB Stage, Power BJTs, Transformer-Coupled Push-Pull Stages, and Tuned Amplifiers, op-amps.

# Oscillators

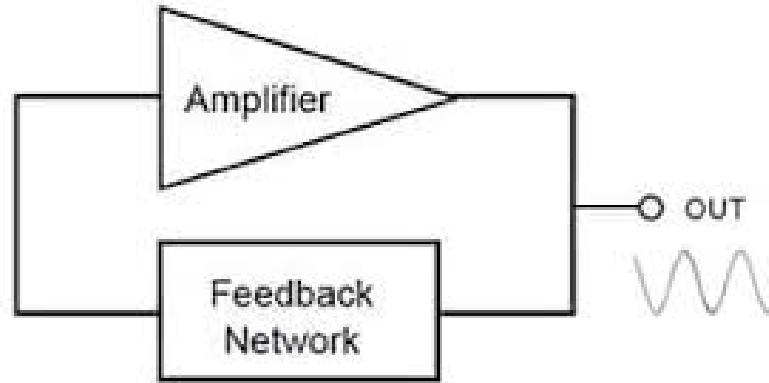

- Oscillators are electric circuits that generate a continuous voltage output waveform at a required single frequency.
- For positive feedback

$$A_f = A/(1-\beta A)$$


1. Sinusoidal Oscillators – these are known as **Harmonic Oscillators** and are generally a “LC Tuned-feedback” or “RC tuned-feedback” type Oscillator that generates a purely sinusoidal waveform which is of constant amplitude and frequency.

2. Non-Sinusoidal Oscillators – these are known as **Relaxation Oscillators** and generate complex non-sinusoidal waveforms that changes very quickly from one condition of stability to another such as “Square-wave”, “Triangular-wave” or “Sawtoothed-wave” type waveforms.

- **Essential condition for oscillation**



**(Barkhausen's Criteria for oscillation) :**

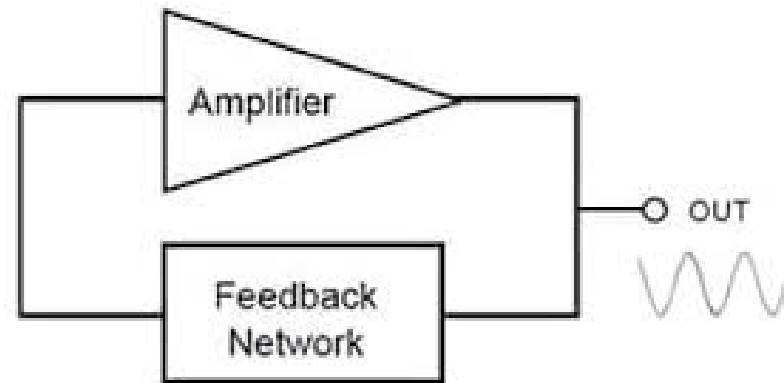1. The loop gain is equal to one in absolute magnitude, which means that  $\beta A = 1$
2. The phase shift through the loop is either zero or an integer multiple of  $2\pi$



- **LC Oscillator :**

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

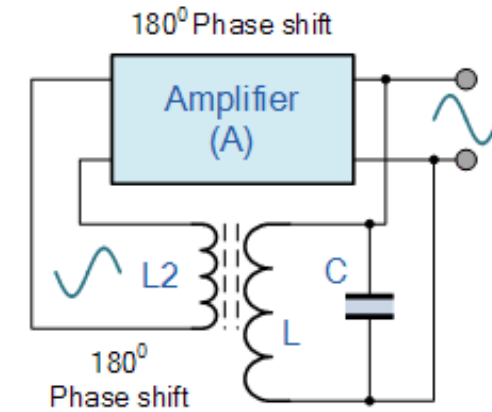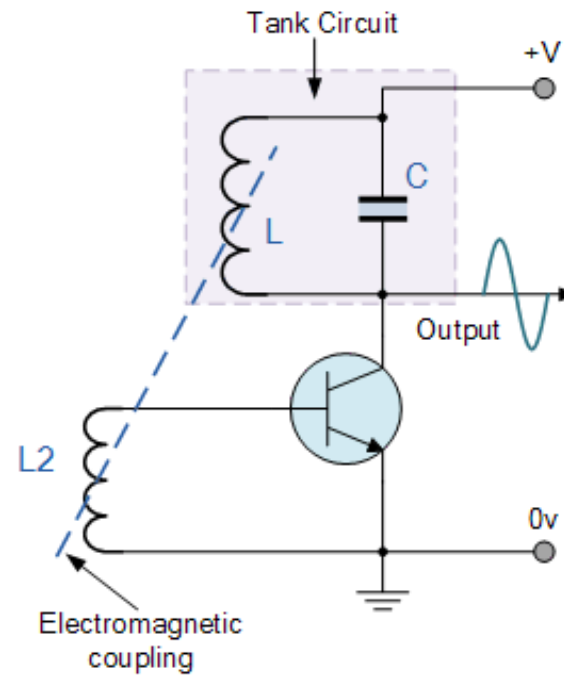


## • Hartley oscillator:

$$f = \frac{1}{2\pi\sqrt{L_T C}}$$

where:  $L_T = L_1 + L_2 + 2M$

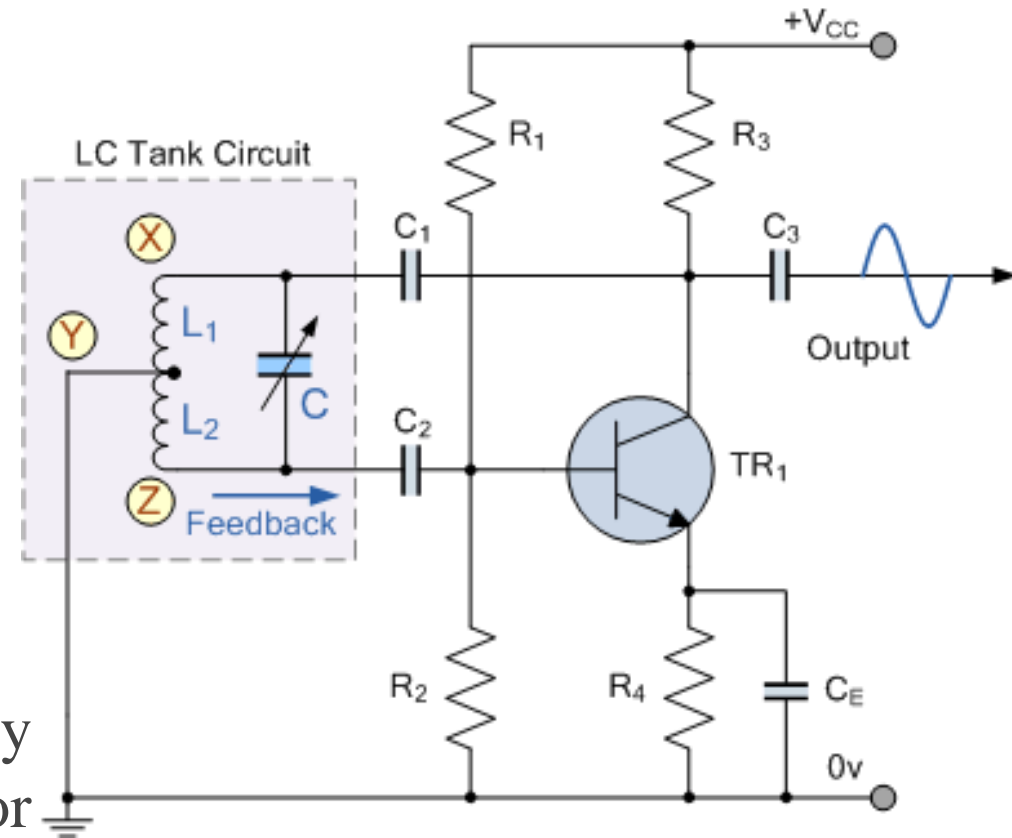- Positive output feedback is inductively coupled by tank circuit consisting inductor coil with center tap.
- It is mainly used as radio receivers.
- It is suitable for oscillations in RF




## • Colpitts oscillator:

$$f_r = \frac{1}{2\pi\sqrt{LC_T}}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{or} \quad C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

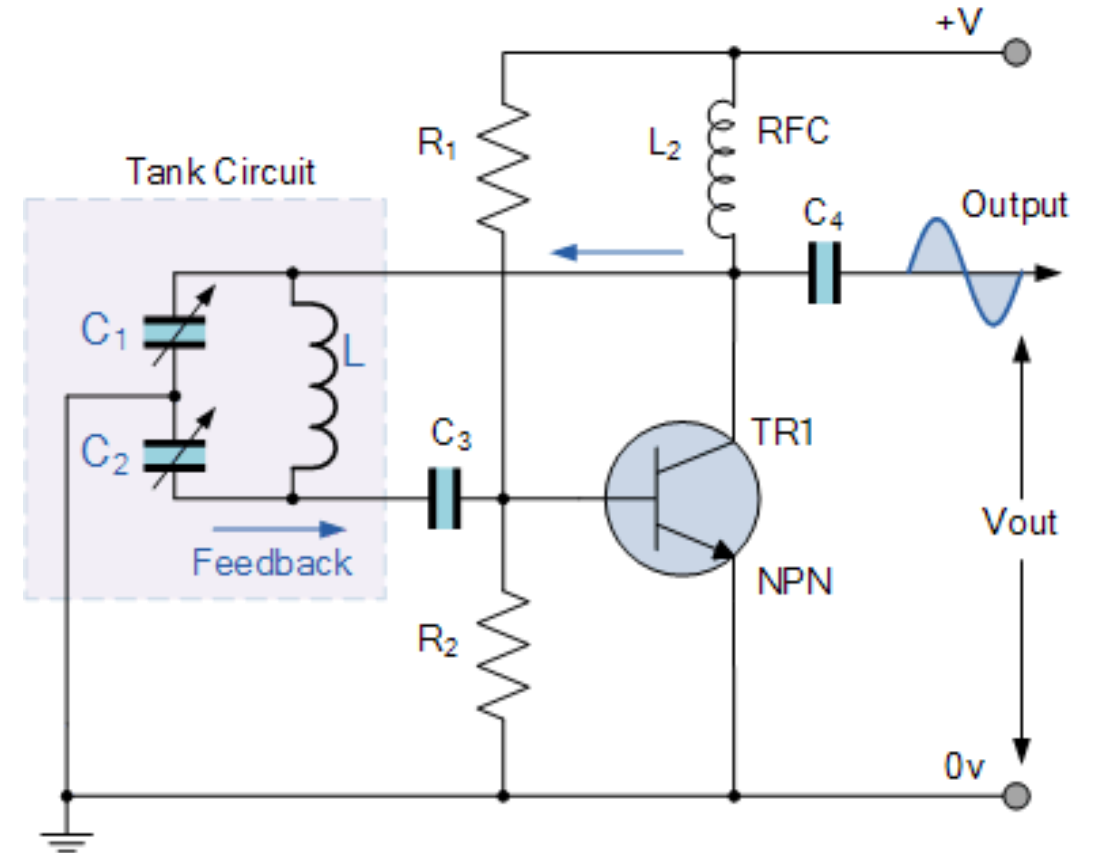
- It consists of a parallel LC resonator tank circuit whose feedback is achieved by way of a capacitive divider
- Used for the generation of sinusoidal output signal with very high frequencies


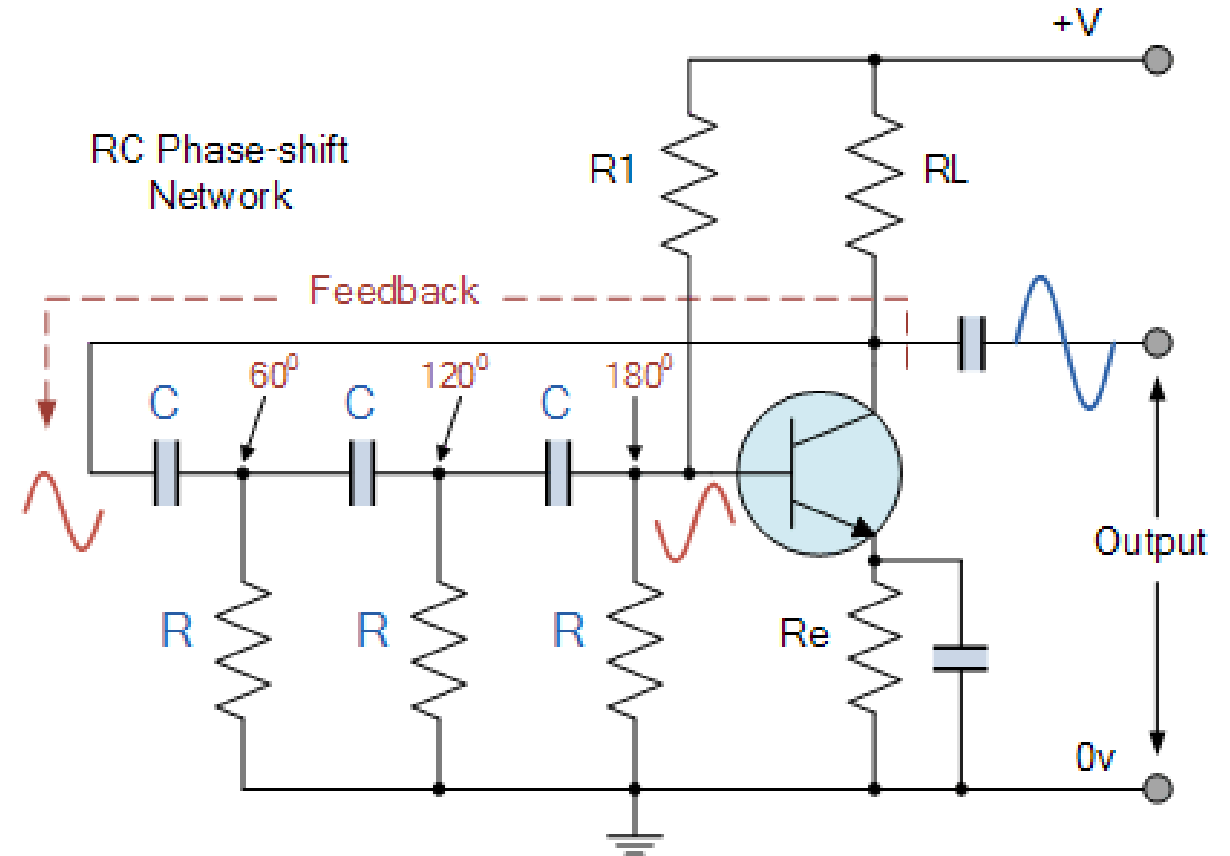
## • RC Phase Shift oscillator:

$$f_r = \frac{1}{2\pi RC\sqrt{2N}}$$

- It is used to generate low or audio frequency signal
- By changing the value of R and C, frequency of oscillator can be changed







- **Wein bridge oscillator:**

$$f_r = \frac{1}{2\pi RC}$$

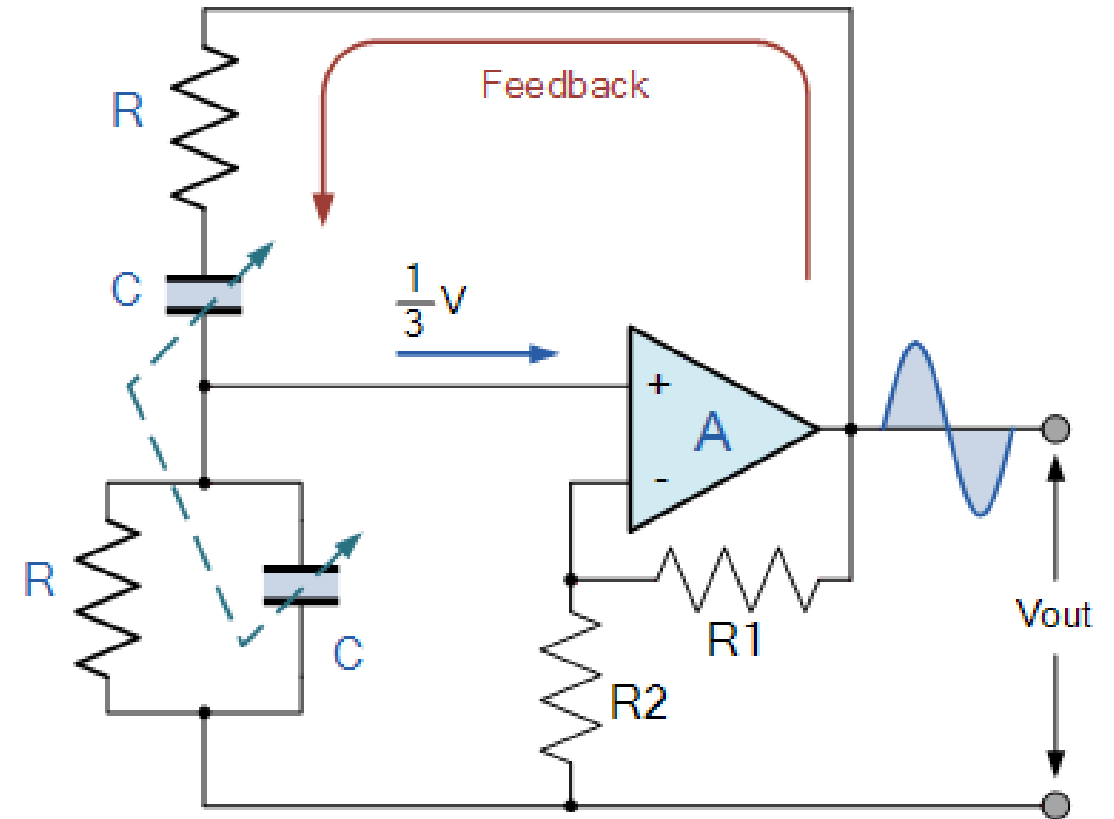- Frequency range: 100Hz to 100 KHz
- Accuracy= 0.1 to 0.5 percent can be achieved
- Used in distortion analyser



## • Crystal oscillator:

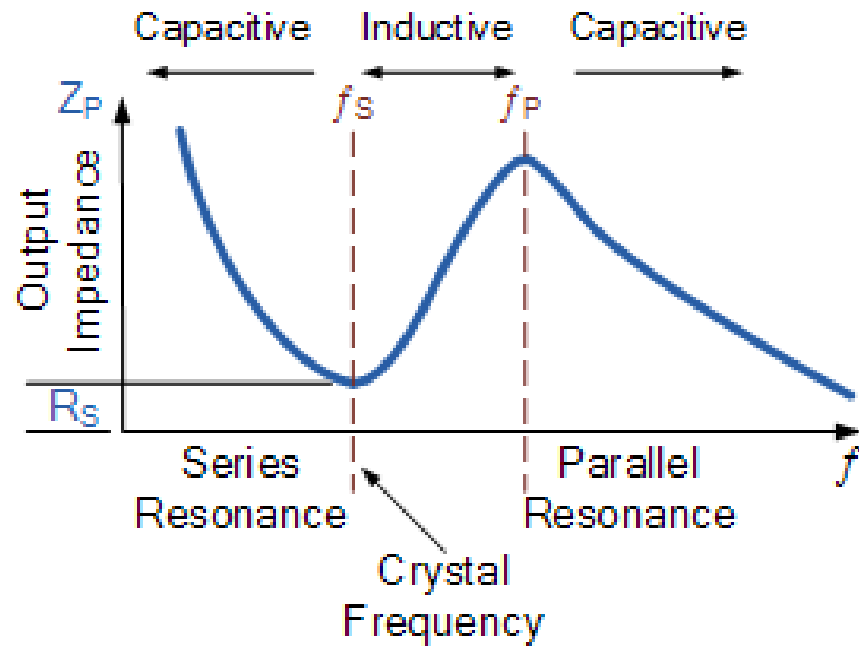


$$R = R \quad \text{and} \quad X_{L_S} = 2\pi f L_S$$

$$X_{C_S} = \frac{1}{2\pi f C_S} \quad \text{and} \quad X_{C_P} = \frac{1}{2\pi f C_P}$$

$$Z_S = \sqrt{R_S^2 + (X_{L_S} - X_{C_S})^2}$$
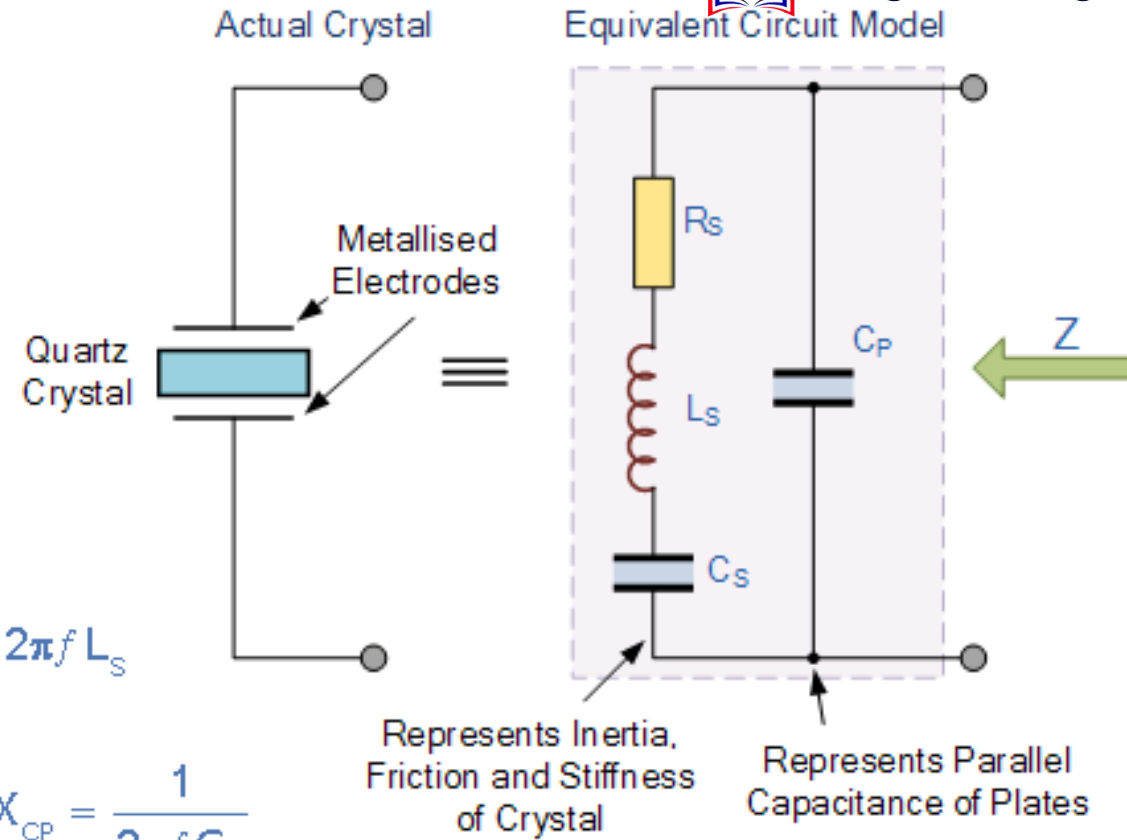
$$\therefore Z_P = \frac{Z_S \times X_{C_P}}{Z_S + X_{C_P}}$$




## • Crystal oscillator:

Series resonant frequency

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}}$$

Parallel resonant frequency
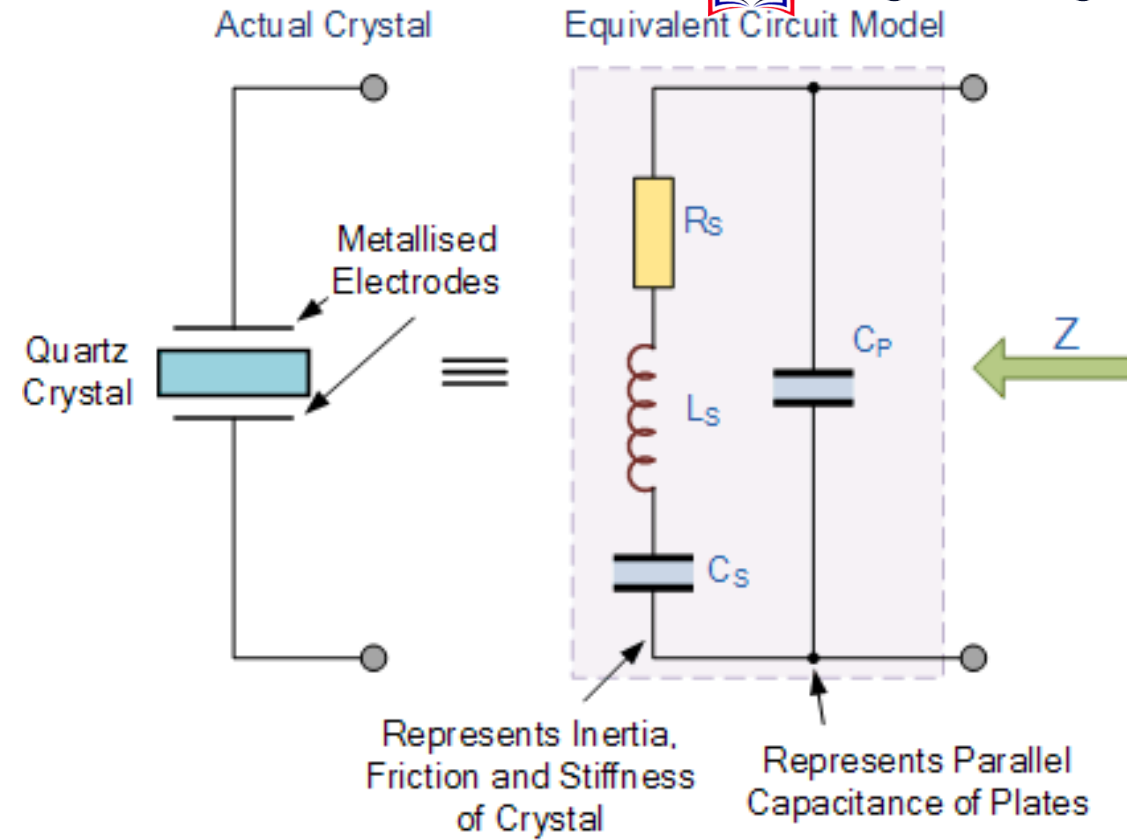
$$f_p = \frac{1}{2\pi\sqrt{L_s \left( \frac{C_p C_s}{C_p + C_s} \right)}}$$




- Crystal oscillator is fixed frequency oscillator with a high Q-factor.
- Crystal oscillator operates on the principle of inverse piezoelectric effect in which alternating voltage applied across the crystal surfaces causes it to vibrate at its natural frequency.
- These vibrations get converted into oscillations
- Crystal like quartz have high Q factor which results in high frequency stability

<i>Type of oscillator</i>	<i>Approximate frequency range</i>
Crystal oscillator	Fixed frequency
Wien bridge oscillator	1 Hz to 1 MHz
Phase-shift oscillator	1 Hz to 10 MHz
Hartley oscillator	10 kHz to 100 MHz
Colpitts oscillator	10 kHz to 100 MHz



# Op Amp

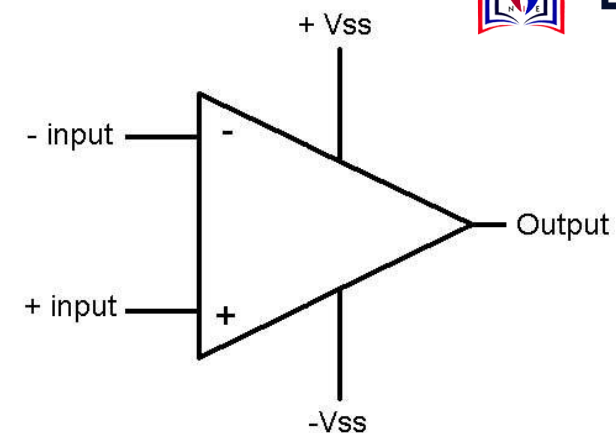

Parameter	Symbol	Ideal Op-Amp	Practical Op-Amp
DC Open loop gain	$A_{OL}$	$\infty$	100 dB
Input Impedance	$Z_{IN}$	$\infty$	2M $\Omega$
Output Impedance	$Z_{out}$	0	75 $\Omega$
Input Offset Voltage	$V_{IO}$	0	1mV
Slew rate	SR	$\infty$	Depends on input signal frequency
Bandwidth	BW	$\infty$	Depends on input signal frequency
CMRR	$\rho$	$\infty$	90 dB

# Tuned Amplifier

- Tuned amplifiers are the amplifiers that are employed for the purpose of **tuning**. Tuning means selecting. Among a set of frequencies available, if there occurs a need to select a particular frequency, while rejecting all other frequencies, such a process is called **Selection**. This selection is done by using a circuit called as **Tuned circuit**.
- When an amplifier circuit has its load replaced by a tuned circuit, such an amplifier can be called as a **Tuned amplifier circuit**.