

**1 Kirchhoff's current law states that**

- (a) net current flow at the junction is positive
- (b) Algebraic sum of the currents meeting at the junction is zero
- (c) no current can leave the junction without some current entering it.
- (d) total sum of currents meeting at the junction is zero

Ans: b

**2. Kirchhoff's current law is applicable to only**

- (a) junction in a network
- (b) closed loops in a network
- (c) electric circuits
- (d) electronic circuits

Ans: a

**3. Thevenin resistance  $R_{th}$  is found**

- (a) by removing voltage sources along with their internal resistances
- (b) by short-circuiting the given two terminals
- (c) between any two 'open' terminals
- (d) between same open terminals as for  $E_{th}$

Ans: d

**4. An ideal voltage source should have**

- (a) large value of e.m.f.
- (b) small value of e.m.f.
- (c) zero source resistance
- (d) infinite source resistance

Ans: c

**5. To determine the polarity of the voltage drop across a resistor, it is necessary to know**

- (a) value of current through the resistor
- (b) direction of current through the resistor
- (c) value of resistor
- (d) e.m.fs. in the circuit

Ans: b

**6. Which of the following is non-linear circuit parameter?**

- (a) Inductance
- (b) Condenser
- (c) Wire wound resistor
- (d) Transistor

Ans: d

**7. For maximum transfer of power, internal resistance of the source should be**

- (a) equal to the load resistance

- (b) less than the load resistance
- (c) more than the load resistance
- (d) none of the above

Ans: a

**8. The circuit whose properties are same in either direction is known as**

- (a) unilateral circuit
- (b) bilateral circuit
- (c) irreversible circuit
- (d) reversible circuit

Ans: b

**9. The circuit has resistors, capacitors and semi-conductor diodes. The circuit will be known as**

- (a) non-linear circuit
- (b) linear circuit
- (c) bilateral circuit
- (d) none of the above

Ans: a

**10. Which of the following is not a nonlinear element?**

- (a) Gas diode
- (b) Heater coil

- (c) Tunnel diode
- (d) Electric arc

Ans: b

**11. Application of Norton's theorem to a circuit yield**

- (a) equivalent current source and impedance in series
- (b) equivalent current source and impedance in parallel
- (c) equivalent impedance
- (d) equivalent current source

Ans: b

**12. Kirchhoff's current law states that**

- (a) net current flow at the junction is positive
- (b) Algebraic sum of the currents meeting at the junction is zero
- (c) no current can leave the junction without some current entering it
- (d) total sum of current meeting at the junction is zero

Ans: b

**13. The superposition theorem is applicable to**

- (a) voltage only
- (b) current "only
- (c) current and voltage

(d) current, voltage and power

Ans: c

**14. Between the branch voltages of a loop the Kirchhoff s voltage law imposes**

- (a) non-linear constraints
- (b) linear constraints
- (c) no constraints
- (d) none of the above

Ans: b

**15. While calculating  $R_{th}$  in Thevenin's theorem**

- (a) all independent sources are made dead
- (b) only current sources are made dead
- (c) only voltage sources are made dead
- (d) all voltage and current sources are made dead

Ans: a

**17. The superposition theorem requires as many circuits to be solved as there are**

- (a) sources, nodes and meshes
- (b) sources and nodes
- (c) sources
- (d) nodes

Ans: c

**18. According to KVL, the algebraic sum of all IR drops and emf in any closed loop of a network is always**

- (a) negative
- (b) positive
- (c) determined by battery emf
- (d) zero

Ans: d

**19. KCL is applicable to only**

- (a) junction in a network
- (b) closed loops in a network
- (c) electric circuits
- (d) electronics circuit

Ans : a

**20. Superposition theorem can be applied only to circuits having**

- (a) resistive elements
- (b) passive elements
- (c) non linear elements
- (d) linear bilateral elements

Ans : d

**21. The concept on which superposition theorem is based on**

- (a) reciprocity
- (b) duality
- (c) non linearity
- (d) linearity

**22. “Maximum power output is obtained from a network when the load resistance is equal to the output resistance of the network as seen from the terminals of the load”. The above statement is associated with**

- (a) Superposition Theorem
- (b) Thevenin’s Theorem
- (c) Norton’s Theorem
- (d) MPT

**23. For high efficiency of transfer of power, internal resistance of the source should be**

- (a) equal to the load resistance
- (b) less than the load resistance  $= 1 / (1 + R_i/R_L)$
- (c) more than the load resistance
- (d) all of the above

Ans : b

**24. the circuit whose properties are same in either direction is known as**

- (a) Unilateral circuit

- (b) Bilateral circuit
- (c) irreversible circuit
- (d) reversible circuit

Ans : b

**25. the circuit has resistor, capacitor, and semiconductor diodes, the circuit will be known as**

- (a) non linear
- (b) linear
- (c) bilateral
- (d) all of the above

Ans : a

**26. the superposition theorem is applicable to**

- (a) linear, non linear, and time variant response
- (b) linear and non linear resistors only
- (c) linear response only
- (d) none of the above

Ans : c

**27. Application of Norton's theorem to a circuit yields**

- (a) equivalent current source and impedance in series
- (b) equivalent current source and impedance in parallel



- (c) equivalent voltage source and impedance in parallel
- (d) equivalent current source only



Nepal Institute of  
Engineering